
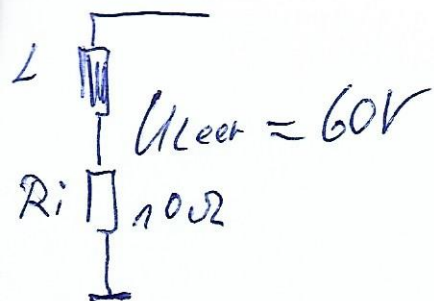


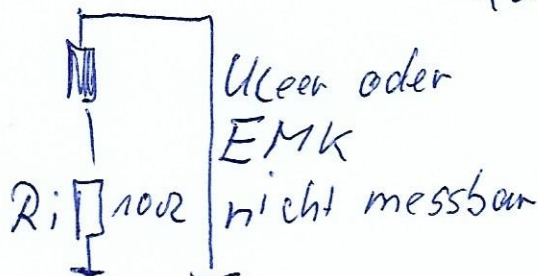


$$I = 0 \quad P = 0$$

Kurzschlussleistung



$$I = \frac{U_{Leer}}{R_i + 0} = \frac{60V}{100\Omega} = 6A$$

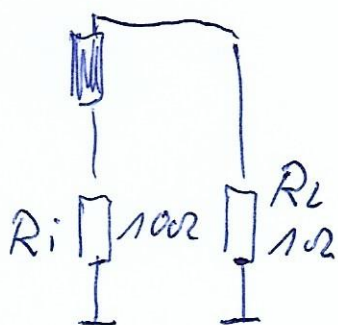
$$P_{R_i} = I^2 \cdot R_i = 36 \cdot 100\Omega = \underline{\underline{360W}}$$



$$I = \frac{U_{Leer}}{R_i + R_L} = \frac{60V}{100\Omega + 10\Omega} = 5,45A$$

$$P_{R_i} = I^2 \cdot R_i = 29,75 \cdot 100\Omega = 297,5W$$
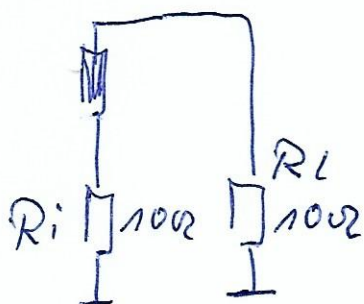
$$P_L = I^2 \cdot R_L = 29,75 \cdot 10\Omega = 29,75W$$




$$I = \frac{U_{Leer}}{R_i + R_L} = \frac{60V}{100\Omega + 100\Omega} = 3A$$

$$P_{R_i} = I^2 \cdot R_i = 9 \cdot 100\Omega = 90W$$

$$P_L = I^2 \cdot R_L = 9 \cdot 100\Omega = \underline{\underline{90W}}$$

Optimal

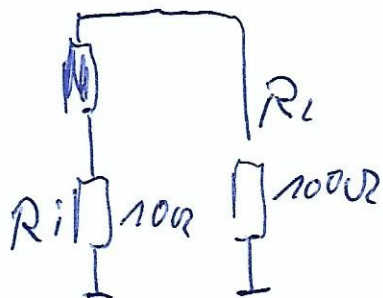

$$I = \frac{U_{Leer}}{R_i + R_L} = \frac{60V}{100\Omega + 1000\Omega} = 0,545A$$

$$P_{R_i} = I^2 \cdot R_i = 0,2975 \cdot 100\Omega = 29,75W$$

$$P_L = I^2 \cdot R_L = 0,2975 \cdot 1000\Omega = 29,75W$$

nutzbare Leistung an R_L max 90W $\frac{1}{4}$
 Kurzschlussleistung an R_i 360W